IC 7805 vs LM2596

Operating Principles, Electrical Limits, Thermal Behaviour and USB Charging-Current Considerations

Technical research reference | 6 November 2026

Safety and scope: This report explains regulator behaviour and interprets manufacturer and USB specifications. It is not a mains-power construction guide. Mains circuitry can cause fatal electric shock and fire. Do not build, probe or modify a mains-connected supply. Educational experiments should use a certified, isolated, enclosed low-voltage DC source with appropriate adult/professional supervision.

Abstract

The 7805 and LM2596 can both provide a nominal 5 V rail, but use fundamentally different regulation methods. The 7805 is a linear series regulator: it controls output voltage by varying the voltage dropped across an internal pass element, so the difference between input and output is dissipated mainly as heat. The LM2596 is a switching step-down (buck) regulator: it switches energy into an inductor and filters the resulting waveform to obtain a lower DC output. Its switching approach can provide substantially better efficiency when the input voltage is appreciably above 5 V. Neither regulator, by itself, defines how much current a USB-connected device is allowed to draw. That depends on the port's current capability, connector/cable and charging identification or negotiation standard.

1. Executive comparison

Property	7805 family (5 V fixed)	LM2596
Method	Linear series regulation	Switch-mode buck conversion
Output	Nominal 5 V	5 V fixed version; adjustable version available
Input	Needs input above output by dropout margin; TI family absolute maximum input 35 V	4.5–40 V operating input range
Current	Family can exceed 1.5 A with suitable thermal design; practical output capability limited	3 A rated output capability, subject to datasheet conditions and external compo
Frequency	No switching frequency	150 kHz fixed-frequency oscillator
Main losses	Approximately (VIN–VOUT)×IOUT	Switch, diode, inductor, capacitor and control losses
External parts	Bypass capacitors; heatsink may be required	Inductor, catch diode, input/output capacitors; feedback network for adjustable
Best suited to	Small voltage difference and modest current	Larger voltage reduction where efficiency matters

Headline current ratings are not unconditional guarantees. Package, junction temperature, input voltage, heat dissipation, inductor/diode selection, PCB copper and airflow determine usable continuous current.

2. 7805 linear regulator

2.1 Operating principle

The 7805 is a fixed positive-voltage linear regulator. Internally, a voltage reference and error amplifier compare a representation of the output voltage against the reference. The control circuit adjusts an internal series pass transistor to keep the output close to 5 V as input voltage and load current vary within the specified range.

```
VOUT → feedback sensing → error amplifier/reference → pass transistor → VOUT
```

If the output falls as load current increases, the control loop increases pass-element conduction. If the output rises, it reduces conduction. Unlike a buck converter, the 7805 does not store and transfer energy through an inductor; it drops excess voltage across the pass element.

2.2 Input headroom and dropout

A linear regulator requires its input to remain sufficiently above its output. A useful approximation is:

```
VIN(min) ≈ VOUT + Vdropout
```

The TI LM340/LM7805 family datasheet gives a dropout voltage around 2 V under a stated 1 A test condition. Thus, a 5 V output generally requires roughly 7 V or more at the regulator input under that test condition. The exact requirement varies with load, temperature, manufacturer and device variant. Do not treat 2 V as universal.

2.3 Power dissipation

The pass element dissipates approximately:

```
PD ≈ (VIN − VOUT) × IOUT
```

At 12 V input, 5 V output and 0.5 A:

```
PD ≈ (12 − 5) × 0.5 = 3.5 W
```

At 1 A, the same condition gives approximately 7 W. This is substantial heat for a small package without an adequate thermal path.

```
TJ ≈ TA + PD × RθJA
```

Here TA is ambient temperature and RθJA is the effective junction-to-ambient thermal resistance of the assembled device. A heatsink or improved thermal path can reduce effective thermal resistance, but the actual value depends on mounting, PCB and airflow. Thermal shutdown is protection, not a normal operating mode.

2.4 Current capability and protection

TI's LM340/LM7805 family documentation describes output capability above 1.5 A with suitable thermal considerations. It also documents internal current limiting, thermal shutdown and safe-operating-area protection. A typical family current-limit value is around 2.4 A; this is a protection threshold, not a recommended continuous output current.

• A module advertised as “7805 1.5 A” may not sustain 1.5 A continuously in a compact assembly.

• Calculate dissipation at maximum input voltage and expected load current.

• Current limiting and thermal shutdown do not replace upstream protection or a safe enclosure.

2.5 Strengths and limitations

• Strengths: simple, inexpensive, low circuit complexity and no switching-frequency ripple.

• Limitations: poor efficiency when VIN is much greater than 5 V; heat rises with voltage drop and load current; input must remain above dropout.

3. LM2596 buck converter

3.1 Operating principle

The LM2596 is a monolithic fixed-frequency step-down switching regulator. TI specifies a 4.5–40 V input range, 3 A output-current capability and 150 kHz oscillator. Variants include fixed 3.3 V, 5 V and 12 V outputs and an adjustable version.

A buck converter controls the average energy delivered to the output by switching an internal power transistor on and off. The inductor stores energy while the switch is on and releases energy while it is off. In the classic LM2596 topology, a catch diode provides the inductor-current path during the off interval. The output capacitor smooths the resulting current into a relatively steady DC output.

3.2 Switching cycle

• Switch ON: the internal switch connects the input to the inductor path. Inductor current rises and energy is stored in its magnetic field; the source also supplies the load.

• Switch OFF: the switch opens. Inductor current continues in the same direction through the catch diode and load, while the inductor releases stored energy.

• Filtering: the output capacitor supplies or absorbs the difference between inductor current and load current, reducing output-voltage ripple.

The control circuit senses output voltage through feedback and adjusts switching behaviour to maintain regulation.

3.3 Ideal buck relationship

For an ideal buck converter in continuous-conduction mode:

```
VOUT = D × VIN and D = VOUT / VIN
```

D is the switch duty ratio, between 0 and 1. Real output is affected by switch and diode drops, inductor resistance, ripple, control limits and load.

For ideal conversion from 12 V to 5 V:

```
D ≈ 5/12 ≈ 0.417 (41.7%)
```

3.4 Inductor and capacitor

The inductor opposes rapid changes in current. Its current increases during the switch-on interval and decreases during the off interval while continuing to feed the load. The output capacitor reduces voltage variation caused by pulsed energy transfer. TI's typical application uses an inductor, catch diode, input capacitor and output capacitor. Component values must be selected for the actual input/output conditions; a generic module should not be assumed to meet every ripple, thermal or EMI requirement.

3.5 Efficiency and losses

A switching regulator is generally more efficient than a linear regulator for a large voltage reduction. Losses include internal switch conduction and switching losses, diode forward loss, inductor winding/core loss, capacitor ESR loss and control-circuit consumption.

```
η = POUT / PIN
```

For a 5 V, 1 A output, POUT = 5 W. At an illustrative 85% efficiency:

```
PIN = 5/0.85 ≈ 5.88 W; PLOSS ≈ 0.88 W
```

85% is an example, not a guaranteed LM2596 efficiency. Actual efficiency depends on operating conditions and must be taken from relevant datasheet curves or measurement.

3.6 Protection and limitations

The LM2596 includes current limiting, thermal shutdown and an ON/OFF control input. TI describes a two-stage frequency-reducing current limit and overtemperature shutdown. These features do not make an incorrectly designed supply safe.

• Switching layouts require careful high-current loop and grounding design to limit ringing and EMI.

• The catch diode, inductor, capacitors and PCB copper must be rated for expected currents and temperatures.

• The IC's 3 A capability does not guarantee that a low-cost module can deliver 3 A continuously.

4. Thermal and efficiency comparison

4.1 7805 at 12 V to 5 V, 1 A

```
POUT = 5 × 1 = 5 W
```

```
PLOSS ≈ (12 − 5) × 1 = 7 W
```

Approximately 7 W must be dissipated as heat, excluding small additional terms. This is a demanding thermal condition and makes the 7805 unattractive for this conversion unless the thermal design is substantial.

4.2 LM2596 illustrative estimate

```
At η = 85%: PIN ≈ 5/0.85 = 5.88 W
```

```
PLOSS ≈ 5.88 − 5 = 0.88 W
```

The switching converter's loss is much lower in this illustrative case. Exact efficiency depends on the IC, external components, layout, operating point and temperature.

4.3 Interpretation

For a DC input substantially higher than 5 V, a buck converter is normally more suitable than a 7805. A 7805 may be reasonable when voltage difference and load current are small and thermal dissipation is demonstrably acceptable.

5. USB output current and charging standards

A 5 V regulator establishes a voltage rail; it does not advertise a USB charging current. The connected device determines its permitted draw by interpreting the port type and charging protocol. The supply must also maintain its output voltage at that current.

Port type	Nominal VBUS	Current figure	Qualification
USB 2.0 SDP	5 V	Up to 500 mA	Host enumeration/configuration rules apply; initial draw is more restricted.
USB 3.x SDP	5 V	Up to 900 mA	USB 2.0 devices remain subject to USB 2.0 limits.
BC1.2 DCP/CDP	5 V	Up to 1.5 A	Requires BC1.2-compatible detection; DCP is charging-only, CDP supports data.
USB Type-C current advertisement	5 V	Default / 1.5 A / 3 A	Current is advertised on CC pins; compliant Type-C source and suitable cable required.
USB Power Delivery	Negotiated	Higher power profiles possible	Requires PD communication/controller and compliant power path; a 5 V regulator alone

5.1 Standard downstream ports

USB-IF compliance guidance specifies a maximum of 500 mA for a standard USB 2.0 downstream port and 900 mA for a standard USB 3.0 downstream port. A standard downstream port is not the same as a dedicated wall charger: host enumeration and configuration rules apply.

5.2 Battery Charging 1.2

BC1.2 distinguishes Standard Downstream Ports (SDP), Charging Downstream Ports (CDP) and Dedicated Charging Ports (DCP). Microchip's technical summary describes DCP and CDP charging capability up to 1.5 A. A DCP does not provide USB data; a CDP can provide data and charging. A device must detect the charging-port signature before drawing the corresponding current.

5.3 USB Type-C and USB Power Delivery

USB Type-C uses Configuration Channel (CC) pins to advertise source current at 5 V. Recognised current advertisements include default USB current, 1.5 A and 3 A. USB Power Delivery is a separate negotiated protocol for other voltage/current profiles. A USB-C receptacle connected to a 5 V regulator does not automatically implement Type-C source advertisement or USB-PD.

5.4 Current targets

• 500 mA: USB 2.0 SDP ceiling, subject to host rules.

• 900 mA: USB 3.x SDP ceiling, subject to the applicable specification.

• Up to 1.5 A: possible with a correctly implemented BC1.2 charging port.

• 1.5 A or 3 A at 5 V: possible for a compliant Type-C source advertising the corresponding current, with an adequately rated power path and cable.

These values are not interchangeable. Do not assume a device will accept the maximum current merely because the regulator can supply it. Port identification must follow the relevant specification.

6. Design interpretation for a 5 V charger

Choose the regulator using the actual DC input range at the regulator, not only the nominal transformer rating. The input must remain within the IC's operating limits during ripple peaks, no-load conditions and transients.

For a buck regulator, the design review must account for input range, output current, inductor saturation/current rating, diode rating, capacitor ripple-current rating, output ripple and thermal behaviour. For a 7805, calculate worst-case dissipation at maximum input voltage and maximum continuous load, then check junction temperature.

The USB port also needs correct charging identification, current limiting, short-circuit and overvoltage protection, suitable connector/cable ratings and stable output under load. Regulator current rating alone is not a USB port specification.

Safety boundary: the mains/transformer/rectifier subsystem is a separate high-risk system. Do not use a breadboard or exposed wiring for mains voltage, and do not connect ordinary measurement equipment to a mains-referenced circuit. Any mains-powered supply requires certified isolation, enclosure and review by a qualified person.

7. Conclusions

The 7805 and LM2596 regulate voltage using different mechanisms. The 7805 is simple and can suit low-current applications with a small input-output voltage difference, but its dissipation rises as (VIN–5 V)×IOUT. The LM2596 uses 150 kHz switching and an inductor-based buck stage, making it generally more suitable for converting a higher DC input to 5 V at moderate or higher current, provided external components and PCB layout are correctly designed.

Neither device alone determines USB charging current. USB 2.0 SDP, USB 3.x SDP, BC1.2 and Type-C use distinct current rules and identification/advertisement mechanisms.

8. Key specifications

Parameter	7805 / LM340 family	LM2596
Nominal output	5 V fixed	5 V fixed variant; adjustable family
Input	Family absolute maximum up to 35 V; requires headroom	4.5–40 V operating range
Output current	Above 1.5 A with suitable thermal design (family datasheet)	3 A rated output capability
Dropout/headroom	About 2 V at stated 1 A test condition in TI data	Buck operation; not a linear dropout figure
Switching frequency	N/A	150 kHz
Protection	Current limit, thermal shutdown, safe-area protection	Current limit, thermal shutdown, ON/OFF
Main concern	Heat dissipation	Switching components, ripple, EMI and thermal design

References

1. Texas Instruments, LM340/LM7805 family datasheet, *Wide VIN 1.5-A Fixed Voltage Regulators*, Rev. L. https://www.ti.com/lit/ds/symlink/lm7800.pdf

2. Texas Instruments, *LM2596 SIMPLE SWITCHER 150-kHz 3-A Step-Down Voltage Regulator*, datasheet Rev. G. https://www.ti.com/lit/ds/symlink/lm2596.pdf

3. Texas Instruments, LM2596 product specifications. https://www.ti.com/product/LM2596

4. USB Implementers Forum, USB 2.0 Specification and compliance updates. https://www.usb.org/document-library/usb-20-specification ; https://compliance.usb.org/index.asp?Format=Standard&UpdateFile;=Policies

5. Microchip Technology, Battery Charging with USB — SDP, CDP and DCP overview.
https://developerhelp.microchip.com/xwiki/bin/view/applications/usb/power-delivery/battery-charging/

6. USB Battery Charging Specification 1.2 reference.
https://www.iteh.us/catalog/standards/clc/ba1c693a-5d15-4e84-975f-875a1bf69527/en-62680-3-2013

Data interpretation: Typical, maximum, absolute-maximum and recommended-operating values have different meanings. Verify the exact manufacturer, suffix, package and datasheet revision of the IC used. Modules sold under the same LM2596 name may differ in layout and component ratings.